

Project-1 : Design and Comparison of Adders

Project 1

❖ Due Date

❖ Nov. 4, 19:00 pm

❖ Summary

- ❖ Design ripple carry adder (RCA) and carry look-ahead adder (CLA) using Verilog language.
- ❖ Compare delay and price of the modules using given gate delays and prices.

❖ Submit Form

- ❖ Submit all Verilog files (files with .v extension) and a report file.

Project 1

❖ Implementation Specifics

- ❖ Implement RCA and CLA modules with Verilog language. Modules should be named as 'rca' and 'cla'.
- ❖ The adders should perform 4-bit + 4-bit operation. The module should have two 4-bit inputs, one 4-bit result output, and 1-bit overflow flag output. Subtraction is not required for this project.
- ❖ A sample testbench will be given as 'testbench.v' file and your modules should be compatible with the given testbench.
- ❖ Use only the gates in the following table. You can't use other gates or expressions (4-bit and gate, if-else clause, etc.)

Module	Delay	Price	Module	Delay	Price
Inverter	5ps	2			
2 input AND	20ps	5	3 input AND	30ps	8
2 input OR	20ps	5	3 input OR	30ps	8
2 input NAND	15ps	4	3 input NAND	25ps	7
2 input NOR	15ps	4	3 input NOR	25ps	7
2 input XOR	30ps	7	3 input XOR	45ps	10

Project 1

❖ The sample testbench

```
`timescale 1ns/1ns

module testbench_prj1();
    reg [3:0] a,b;           // 4-bit inputs
    wire [3:0] s_rca,s_cla; // 4-bit sum outputs
    wire o_rca, o_cla;      // 1-bit overflow flags


    rca my_rca(a,b,s_rca,c_rca);
    cla my_cla(a,b,s_cla,c_cla);

    initial begin
        a=5;b=3; #1;        // s=8 (-8), o=1
        a=4;b=-2; #1;       // s=2, o=0
        a=7;b=6; #1;        // s=13 (-3), o=1
        a=8;b=9; #1;        // s=1, o=1
    end

endmodule
```




Project 1

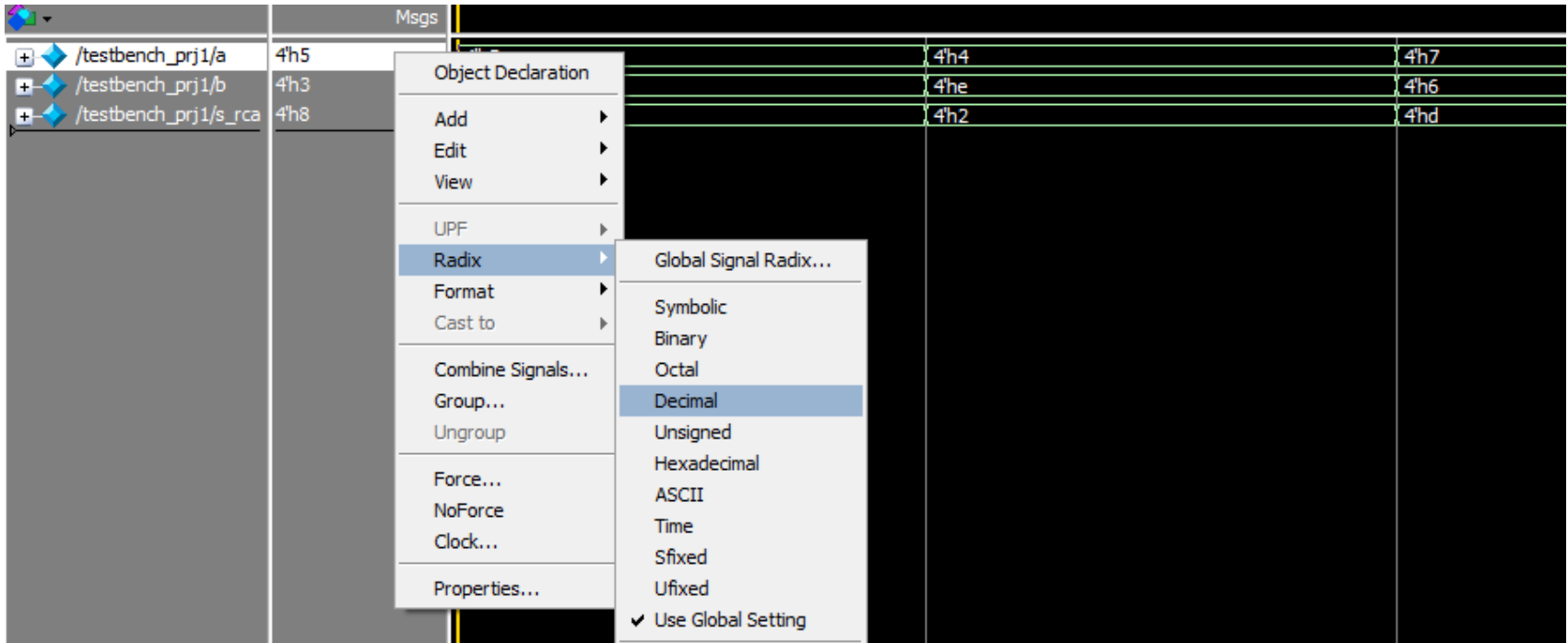❖ Setting Radix






Project 1

❖ Decimal

		Msgs				
+ 	/testbench_prj1/a	4'd5	4'd5	4'd4	4'd7	-4'd8
+ 	/testbench_prj1/b	4'd3	4'd3	-4'd2	4'd6	-4'd7
+ 	/testbench_prj1/s_rca	-4'd8	-4'd8	4'd2	-4'd3	4'd1

❖ Unsigned

+ 	/testbench_prj1/a	4'd5	4'd5	4'd4	4'd7	4'd8
+ 	/testbench_prj1/b	4'd3	4'd3	4'd14	4'd6	4'd9
+ 	/testbench_prj1/s_rca	4'd8	4'd8	4'd2	4'd13	4'd1

Project 1





❖ Analysis Report

- ❖ Calculate and compare the delay and price of the RCA and CLA modules with gate delays and prices in the table above.
- ❖ Take a screenshot of the waveform which expresses the calculated delay.

Project 1

❖ Maximum delay matters

❖ but not all inputs give maximum delays

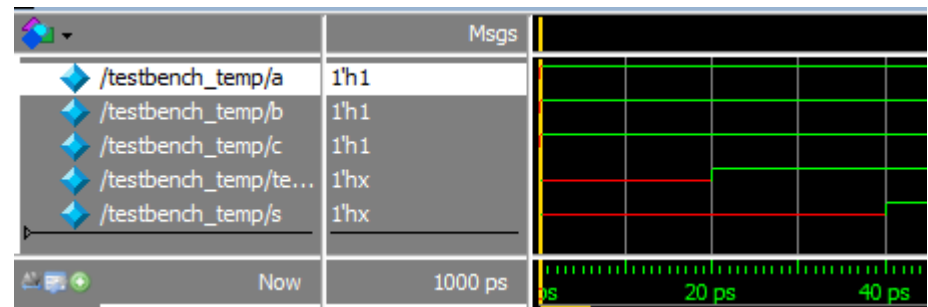 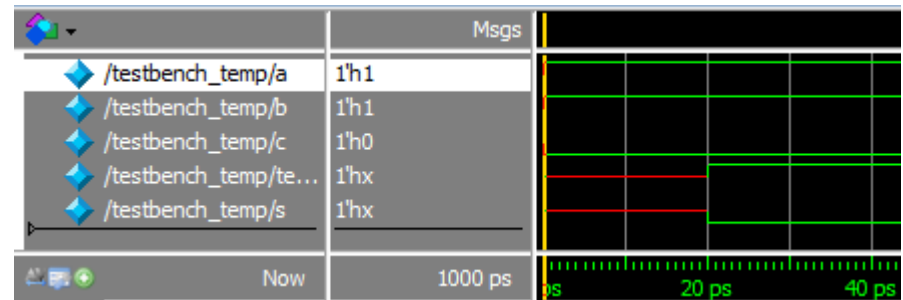 

Q & A

email : dawnshin2000@naver.com